

Implementation Details of Instructions

- **R-Type Instructions**

- ❖ **jr**: I have added another input named "jr" to the control unit. This input is 5_0 bits of instruction. jr is R-type instruction and has unique function code. I check the function code in control unit and if it is jr jump1 becomes "1" and regwrite becomes "0".
- ❖ **nor**: I just updated the alu32 to nor instruction.

- **I-Type Instructions**

- ❖ **addi**: alusrc and regwrite signals must be "1" and aluop must be "0000".
- ❖ **andi**: alusrc and regwrite signals must be "1" and aluop must be "0010".
- ❖ **ori**: alusrc and regwrite signals must be "1" and aluop must be "0011".
- ❖ **bne, beq, bgtz, blez, bltz**: aluop must be "0001" for these instructions. I have added new inputs named c0, c1, c2 to the ALU Control unit to distinguish between these instructions. c2c1c0 = instruction[28-26]. Briefly, I pass the opcodes of these instructions to the ALU Control unit to send a more specific gout signal to the alu32.
- ❖ **bgez**: aluop must be "1001" for this instruction because it's opcode is same with bltz. Difference between them is rt register. So, to check rt I have added new input to the control input which named "rt". I have added aluop3 signal to check only this instruction.

- **J-Type Instructions**

- ❖ **j**: I have added jump0 signal to implement j instruction. If opcode is j instruction opcode, then jump0 signal is "1". So jump1jump0 = 01 and PCSrc multiplexer will send input1 to the out5 wire.
- ❖ **jal**: I have added jump1 signal to implement jal instruction. If instruction is jal instruction then jump1jump0 = 10. In this case, PCSrc multiplexer must send input2 to the out5 wire. Also, memtoreg1 must be "1". Because memtoreg multiplexer must send input2 to the out3. Also, regdest1 must be "1" because we must write to the register ra.


I have needed some multi-bit control lines to implement the instructions. So, I change some parts of control unit in source code.

aluop1, aluop0 -> **aluop3, aluop2, aluop1, aluop0**

I used some 3:1 multiplexers to implement some instructions.

[illegible]

Datapath for Instructions

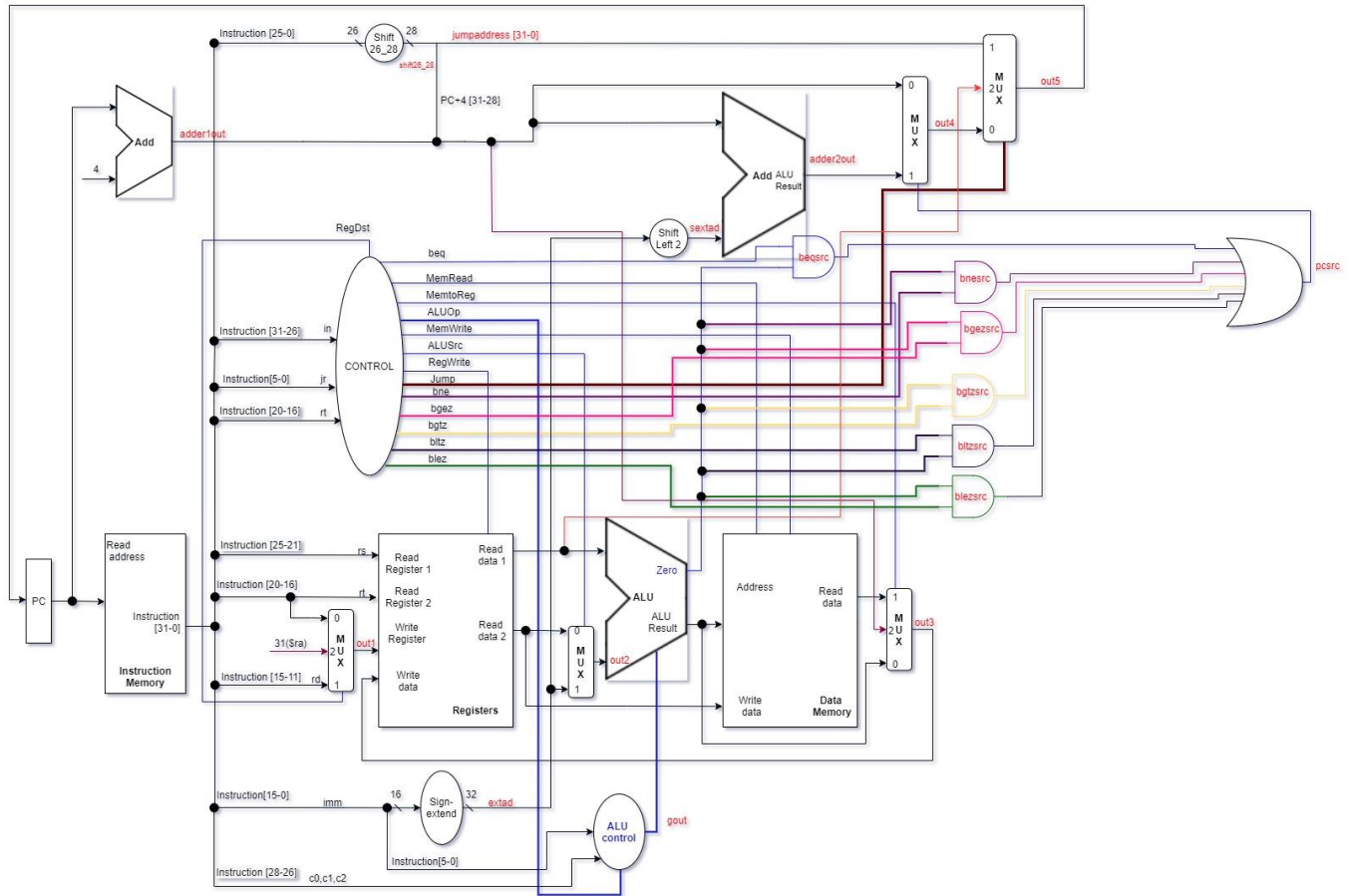

In the code I add comments to explain what I did.